

HomeWork #1

Test 3

a. The main code of project

We can get the expression which I have written on handout from the K-maps. And then we can write code of comparatorExpression module and comparatorGates module.

```
1. module comparatorExpression(A, B, AeqB, AgeqB, AltB );
2. input [1:0] A, B;
3. output AeqB, AgeqB, AltB;
4.
5. //assign AeqB = (A === B);
6. //assign AgeqB = (A >= B);
7. //assign AltB = (A < B);
8.
9. assign AeqB = (~A[0] && ~A[1] && ~B[1] && ~B[0]) || (A[0] && ~A[1] && ~B[1]
&& B[0] || (~A[0] && A[1] && B[1] && ~B[0]) || (A[0] && A[1] && B[1] && B[0]
));
10. assign AgeqB = (A[0] && A[1]) || (A[1] && ~B[1]) || (A[1] && ~B[0]) || (~B[
1] && A[0]) || (~B[1] && ~B[0]);
11. assign AltB = (B[1] && ~A[1]) || (~A[1] && ~A[0] && B[0]) || (~A[0] && B[1]
&& B[0]);
12.
13. endmodule
```


```
1. module comparatorGates(A, B, AeqB, AgeqB, AltB );
2. input [1:0] A, B;
3. output AeqB, AgeqB, AltB;
4. wire aeqU1, aeqU2, aeqU3, aeqU4;
5. wire agaeqU1, agaeqU2, agaeqU3, agaeqU4, ageqU5;
6. wire altU1, altU2, altU3;
7.
8. and aeqU1and(aeqU1,~A[0], ~A[1], ~B[1], ~B[0]);
9. and aeqU2and(aeqU2,A[0], ~A[1], ~B[1], B[0]);
10. and aeqU3and(aeqU3,~A[0], A[1], B[1], ~B[0]);
11. and aeqU4and(aeqU4,A[0], A[1], B[1], B[0]);
```

```


12. or aeqOR(AeqB, aeqU1, aeqU2, aeqU3, aeqU4);
13.
14. and agaeqU1and(agateqU1,~B[0], ~B[1]);
15. and agaeqU2and(agateqU2,~B[1], A[1]);
16. and agaeqU3and(agateqU3,A[1], A[0]);
17. and agaeqU4and(agateqU4,A[1], ~B[0]);
18. and ageqU5and(ageqU5,~B[1], A[0]);
19. or ageqOR(AgeqB, agaeqU1, agaeqU2, agaeqU3, agaeqU4, ageqU5);
20.
21. and altU1and(altU1,B[1], ~A[1]);
22. and altU2and(altU2, ~A[1], ~A[0], B[0]);
23. and altU3and(altU3,~A[0], B[1], B[0]);
24. or altOR(AltB,altU1, altU2, altU3);
25.
26. endmodule

```

b. The RTL of project

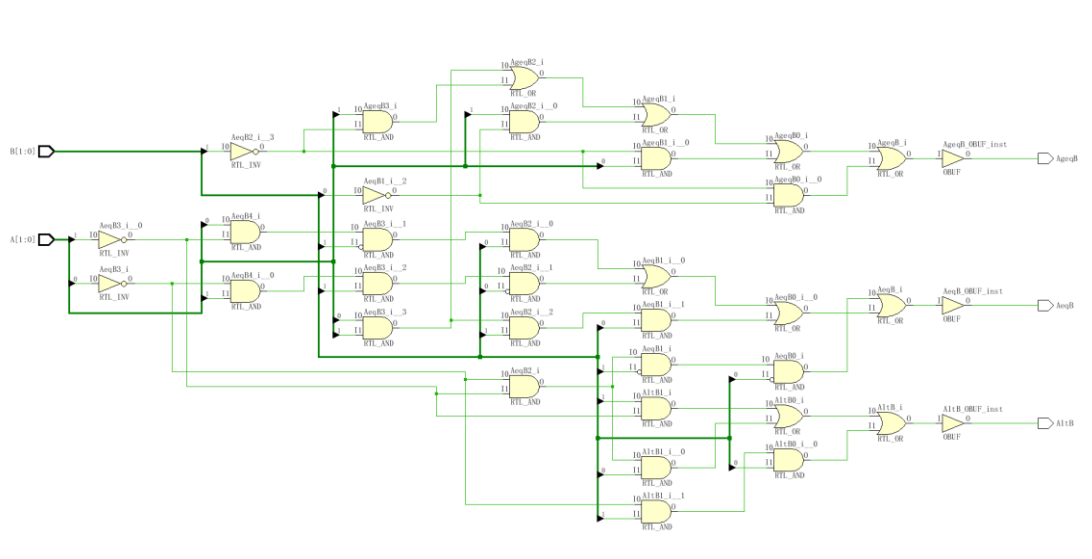

c. The simulation of project

 

Test 4


a. The main code of project

We can easily write the comparator4bit module below through reading test heading.


```
1. module comparator4bit(A, B, AeqB, AgeqB, AltB );
2. input [3:0] A, B;
3. output AeqB, AgeqB, AltB;
4.
5. assign AeqB = (A == B);
6. assign AgeqB = (A >= B);
7. assign AltB = (A < B);
8.
9. endmodule
```

```
1. module comparitor4bits_TB;
2.
3. reg[3:0] A,B;
4. wire AeqBbehavior,AgeqBbehavior,AltBbehavior;
5. comparator4bit UnitBehavior
6. (A,B,AeqBbehavior,AgeqBbehavior,AltBbehavior);
7.
8. initial begin
9.     A=10;B=12;#5;
10.    A=5;B=12;#5;
11.    A=8;B=8;#5;
12.    A=12;B=10;#5;
13.    A=10;B=5;#5;
14.    A=0;B=0;#5;
15.    A=3;B=3;#5;
16.    A=20;B=12;#5;
17.    $stop;
18. end
19. endmodule
```

b. The RTL of project

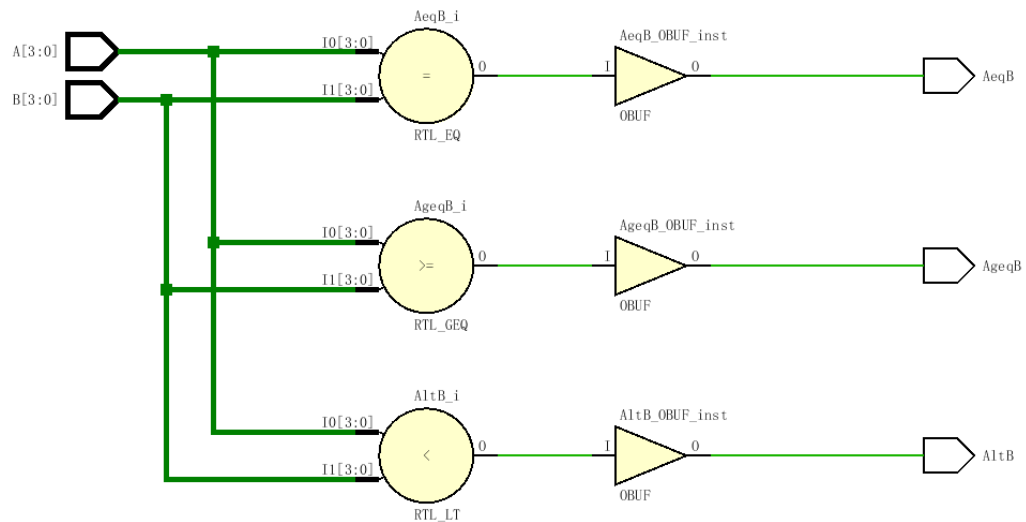

c. The simulation of project

 

Test 8

a. The main code of project

We can know the state machine by the heading and the sample timing sequence, and then we could write a state machine module. Also from that the RTL graph and simulation will come out.


```
1. module statemachine(X, Z, CurrentState, Reset, ClockCycle);
2. input X, Reset, ClockCycle;
3. output reg Z;
4. output reg [2:0] CurrentState;
5. reg [2:0] NextState;
6.
7. parameter Initial = 3'b000, S1 = 3'b001, S10 = 3'b010, S100 = 3'b011, S1001
   = 3'b100;
8.
9. always @(negedge Reset or posedge ClockCycle)begin
10.     if(Reset == 0)
11.         CurrentState <= Initial;
12.     else
13.         CurrentState <= NextState;
14. end
15.
16. always @ (Reset or CurrentState)begin
17.     if(Reset == 0)
18.         Z = 0;
19.     else
20.         case(CurrentState)
21.             Initial: Z = 0;
22.             S1: Z = 0;
23.             S10: Z = 0;
24.             S100: Z = 0;
25.             S1001: Z = 1;
26.             default: Z = 0;
27.         endcase
28.     end
29.
30. always @(X or CurrentState)
31.     begin
```

```

32.         case (CurrentState)
33.             Initial:    NextState = (X==1)?S1:Initial;
34.             S1:         NextState = (X==0)?S10:S1;
35.             S10:        NextState = (X==0)?S100:S1;
36.             S100:       NextState = (X==1)?S1001:Initial;
37.             S1001:      NextState = (X==1)?S1:S10;
38.             default:    NextState = Initial;
39.         endcase
40.     end
41.
42. endmodule

```

b. The RTL of project

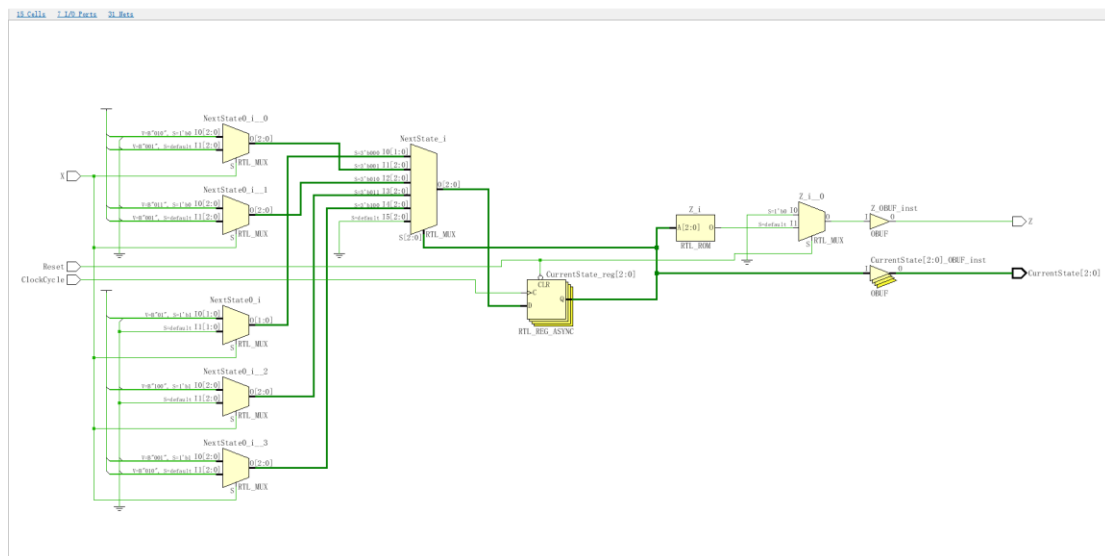

c. The simulation of project

